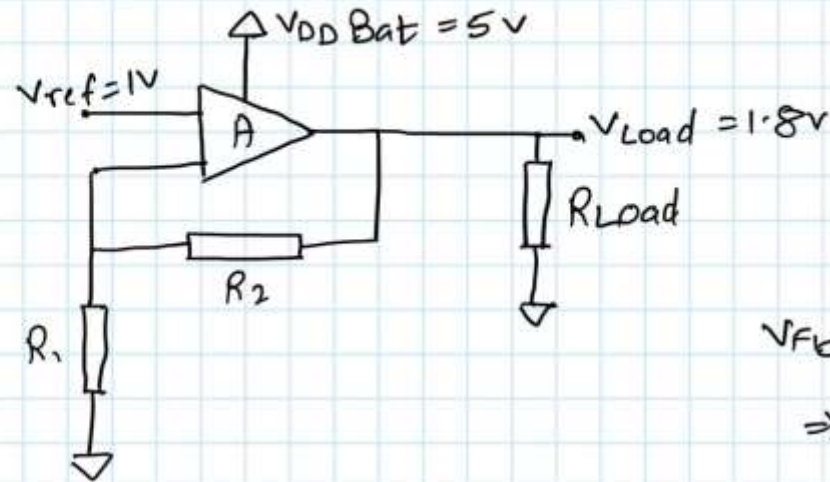


ET4382 - SMPC Mini- Project 1

Raghavendra Joshi 6438180
Daniel Tyukov 5714699

Part A

Part -1:



$$V_{fb} = 1 \text{ when } V_{load} = 1.8$$

$$\Rightarrow \frac{1}{1.8} = \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow \frac{R_2}{R_1} = 0.8$$

So, let's assume $R_1 = 10K$; $R_2 = 8K$


$$\eta = \frac{V_{out}}{V_{in}} \quad [\text{Assuming } I_{out} = I_{in}]$$
$$= \frac{1.8}{5}$$

$$\Rightarrow \boxed{\eta = 0.36} \Rightarrow \text{Quite low} \text{ 😞}$$

So is voltage regulator a good choice?

- NO!
- Efficiency = 0.36
- That's why LDOs have a very low voltage drop - to keep this efficiency high

Schematic for Part A

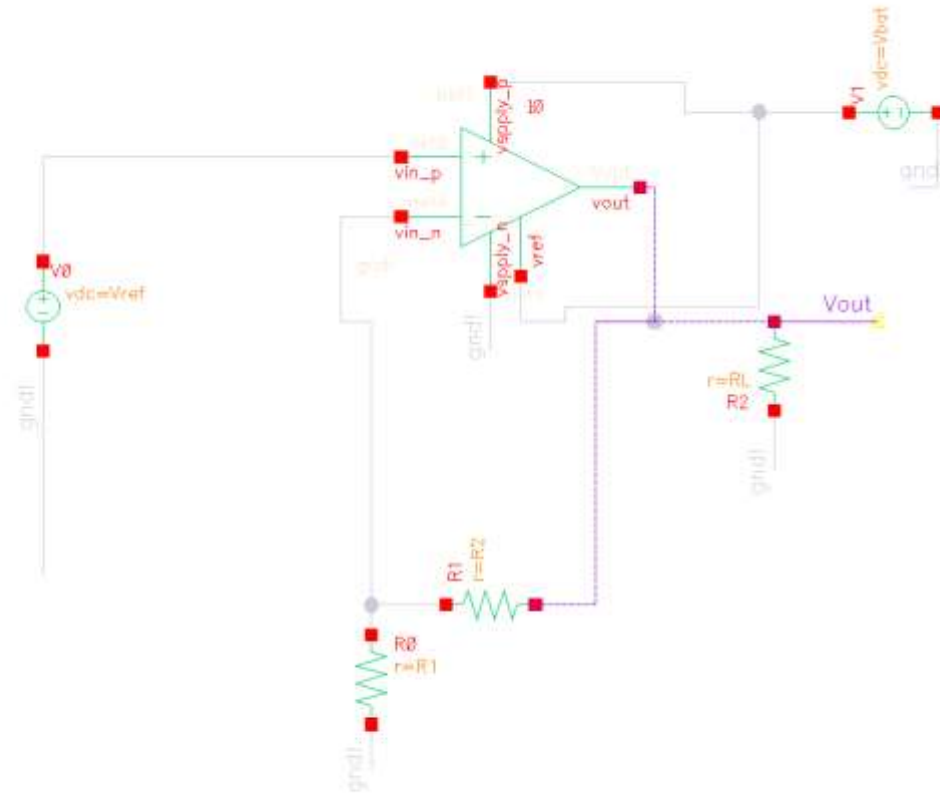


Vout plot for Part A

Transient Response


Thu Apr 2 00:25:45 2026 1

Name	Va
------	----


Vout	
------	--

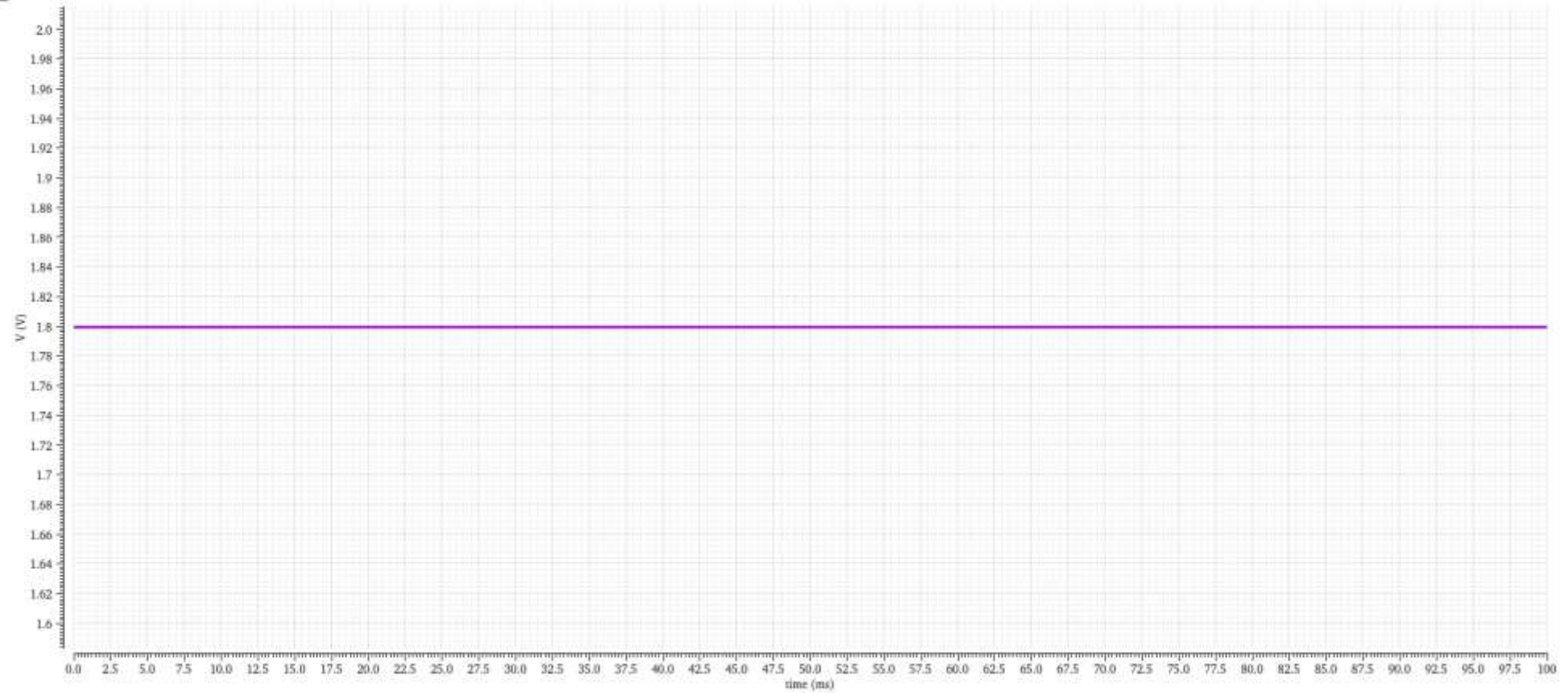


Part B - Schematic

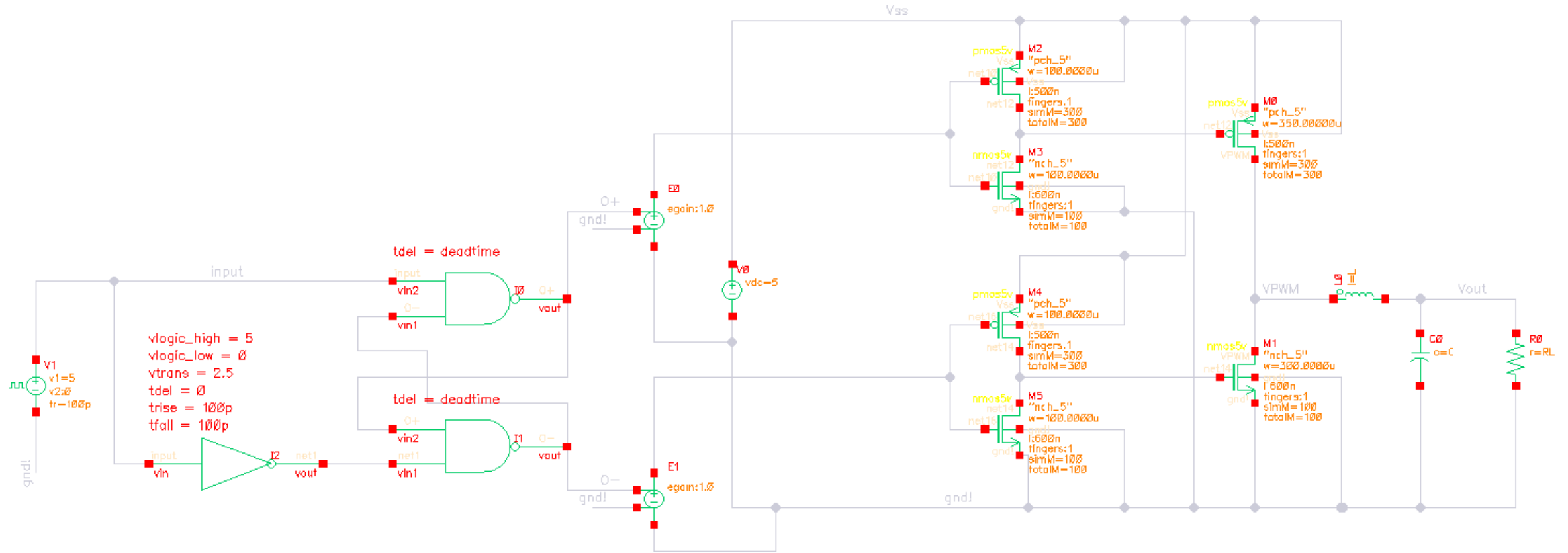

Irripple

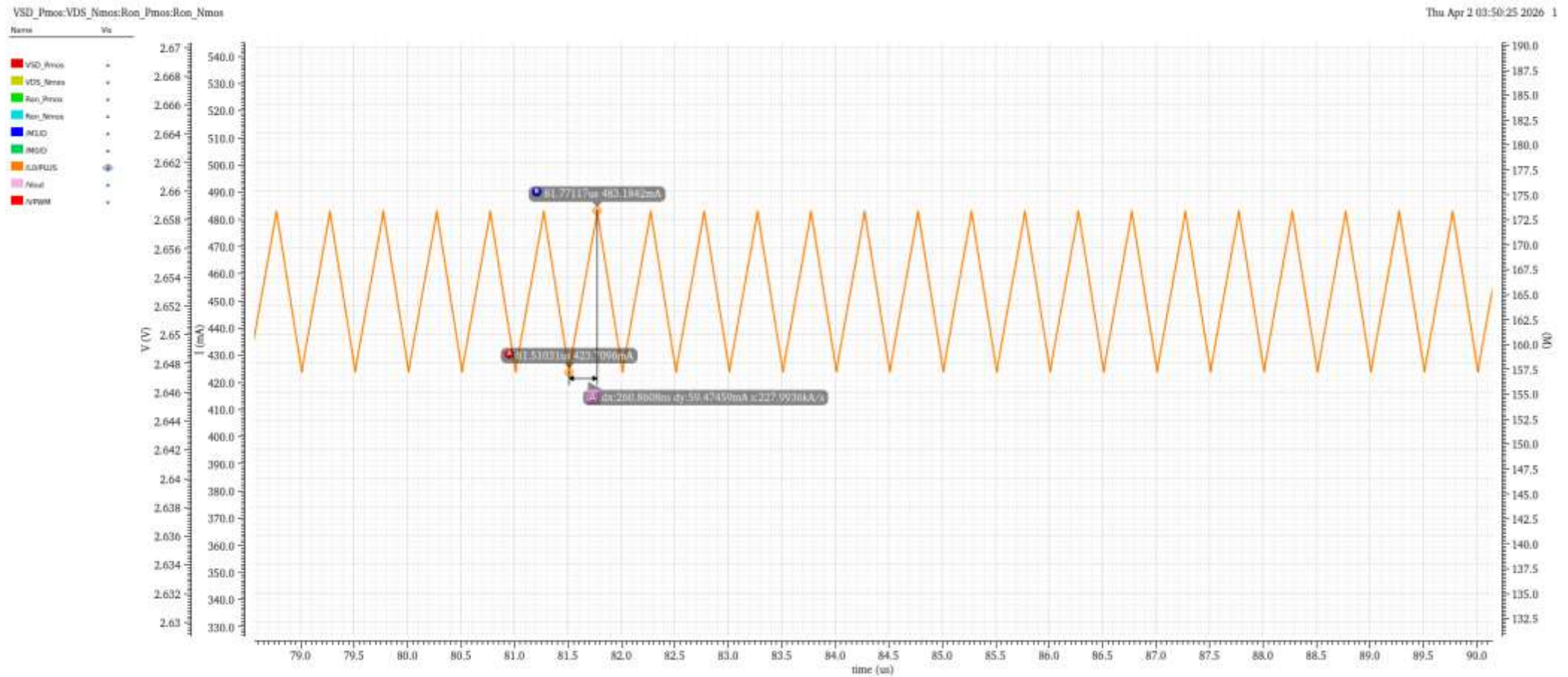

Ron-Nmos

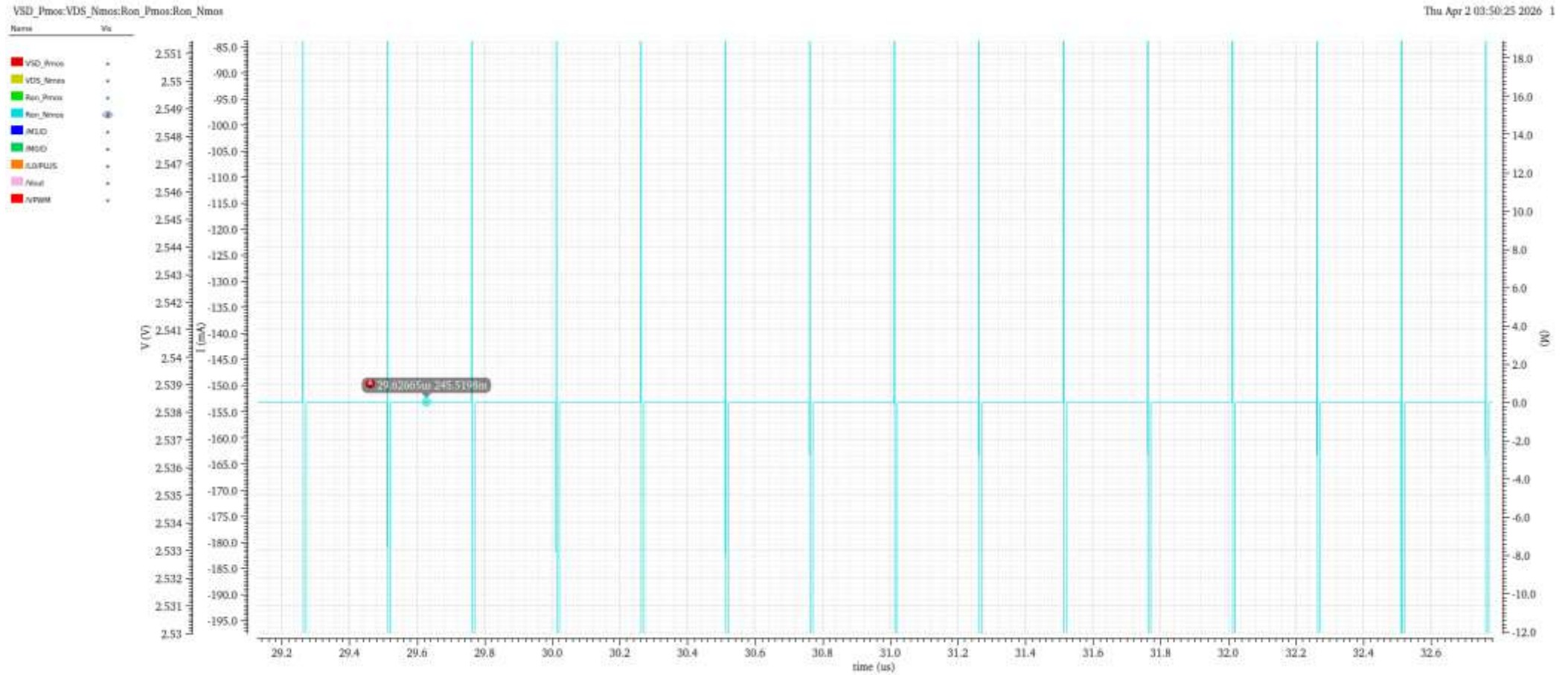


Ron - Pmos

VSD_Pmos:VDS_Nmos:Ron_Pmos:Ron_Nmos

Thu Apr 2 03:50:25 2026 1

Name	Vol
VSD_Pmos	*
VDS_Nmos	*
Ron_Pmos	Ⓢ
Ron_Nmos	*
INLLO	*
MSO	*
ILDPUS	*
Nval	*
NPWM	*

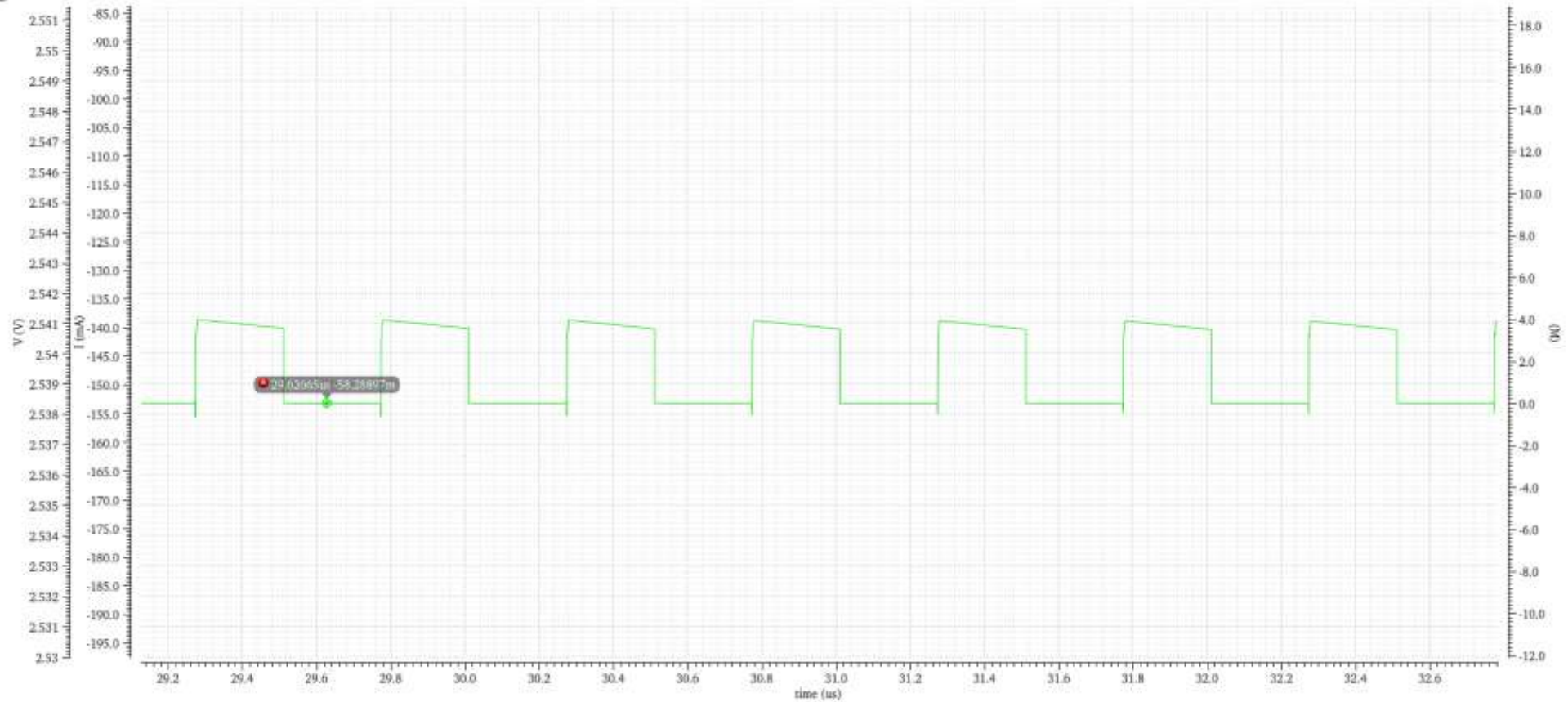

Ron observations

- As I increased the W/L ratios of both the NMOS and PMOS, the extracted on-resistances increased in my simulations.
- The NMOS on-resistance was more sensitive to changes in W/L than the PMOS on-resistance.
- Based on this sizing study, the final device dimensions were chosen as:
 - PMOS: $W/L = 350\ \mu\text{m}/500\ \text{nm}$
 - NMOS: $W/L = 300\ \mu\text{m}/600\ \text{nm}$

Duty Cycle and Ripple Current Calculations

$$\textcircled{1} \text{ Duty Cycle} = \frac{V_O}{V_i} = \frac{1.8}{5} = 0.36$$

$$\text{at } 2\text{MHz}, T = \frac{1}{2 \times 10^6} = 500\text{ns} \Rightarrow t_{\text{on}} = DT = 180\text{ns} \\ \Rightarrow t_{\text{off}} = 320\text{ns}$$

$\textcircled{2}$ Ripple current calc:

$$\text{on-time: } V_L = V_{\text{in}} - V_O = 5 - 1.8 = 3.2\text{V}$$

$$\text{off-time: } V_L = -V_O = -1.8\text{V}$$

$$\text{So, (on-time)} \Delta I_L = \frac{(V_{\text{in}} - V_O)t_{\text{on}}}{L} = \frac{3.2 \times 180\text{n}}{10\mu} = 57.6\text{mA}$$

$$(\text{off-time}) \Delta I_L = \frac{(-1.8) \times 320\text{n}}{10\mu} = -57.6\text{mA} \quad \left. \begin{array}{l} \uparrow \\ \downarrow \end{array} \right\} \text{Ripple current} = 57.6\text{mA}$$

$$I_{\text{avg}} = \frac{V_O}{R_L} = \frac{1.8}{4} = 0.45\text{A}$$

Pcond Loss Calculations (with obtained Ron and I values)

$$P_{\text{cond}} = P_{\text{avg}} + P_{\text{ripple}}$$

$$\begin{aligned} P_{\text{avg}} &= I_{\text{avg}}^2 R_{\text{on,pmos}} \text{Duty} + I_{\text{avg}}^2 R_{\text{on,nmos}} (1-\text{Duty}) \\ &= (455.8 \text{ m})^2 (58.28 \text{ m}) (0.36) \\ &\quad + (455.8 \text{ m})^2 (2454 \text{ m}) (0.64) \\ &= 0.037 \end{aligned}$$

$$\begin{aligned} P_{\text{ripple}} &= I_{\text{ripple}}^2 R_{\text{on,pmos}} \text{Duty} + I_{\text{ripple}}^2 R_{\text{on,nmos}} (1-\text{Duty}) \\ &= (59.47 \text{ m})^2 (58.28 \text{ m}) (0.36) + (59.47 \text{ m})^2 (2454 \text{ m}) (0.64) \\ &= 6.3 \times 10^{-4} \end{aligned}$$

$$P_{\text{cond}} = P_{\text{avg}} + P_{\text{ripple}} = 0.0376 \approx 0.038 \text{ W}$$

$$\begin{aligned} \text{total power} &= I(L_{\text{avg}}) \times V_L \\ &= 455.8 \text{ m} \times 1.8 = 0.82 \text{ W} \end{aligned}$$

$$\frac{P_{\text{cond}}}{P_{\text{total}}} = \frac{0.038}{0.82} \approx 4.63\% \text{ of total power } \therefore$$

$$\boxed{\eta = 0.954}$$

Observations


- P_{cond} is $< 5\%$ of the total power
- I_{avg} matches in simulations and calculations

Transition time plot of VPWM

Transient Response

Thu Apr 2 03:48:00 2026 1


VPWM

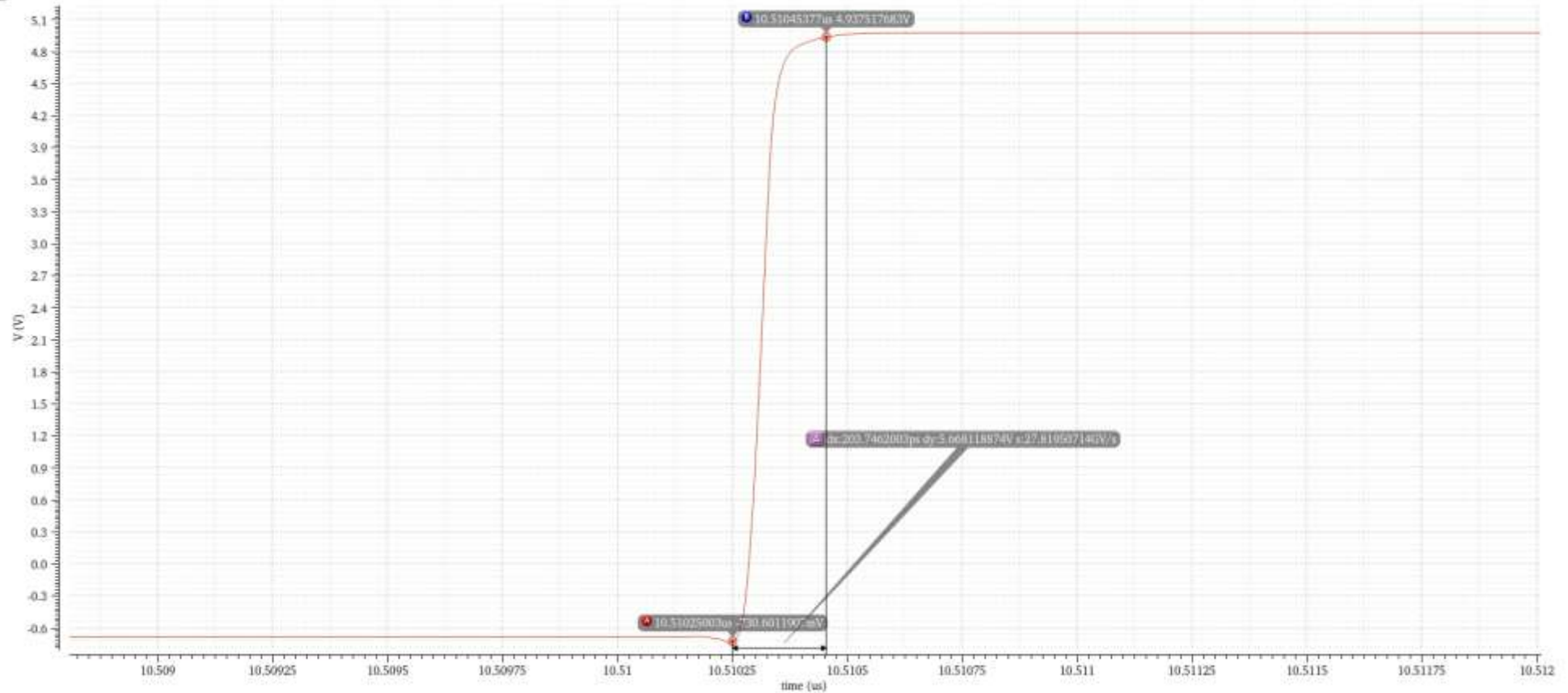

Gate Driver sizes

- Pmos: 100u/500n
- Nmos: 100u/600n
- Transition time < 2.0ns

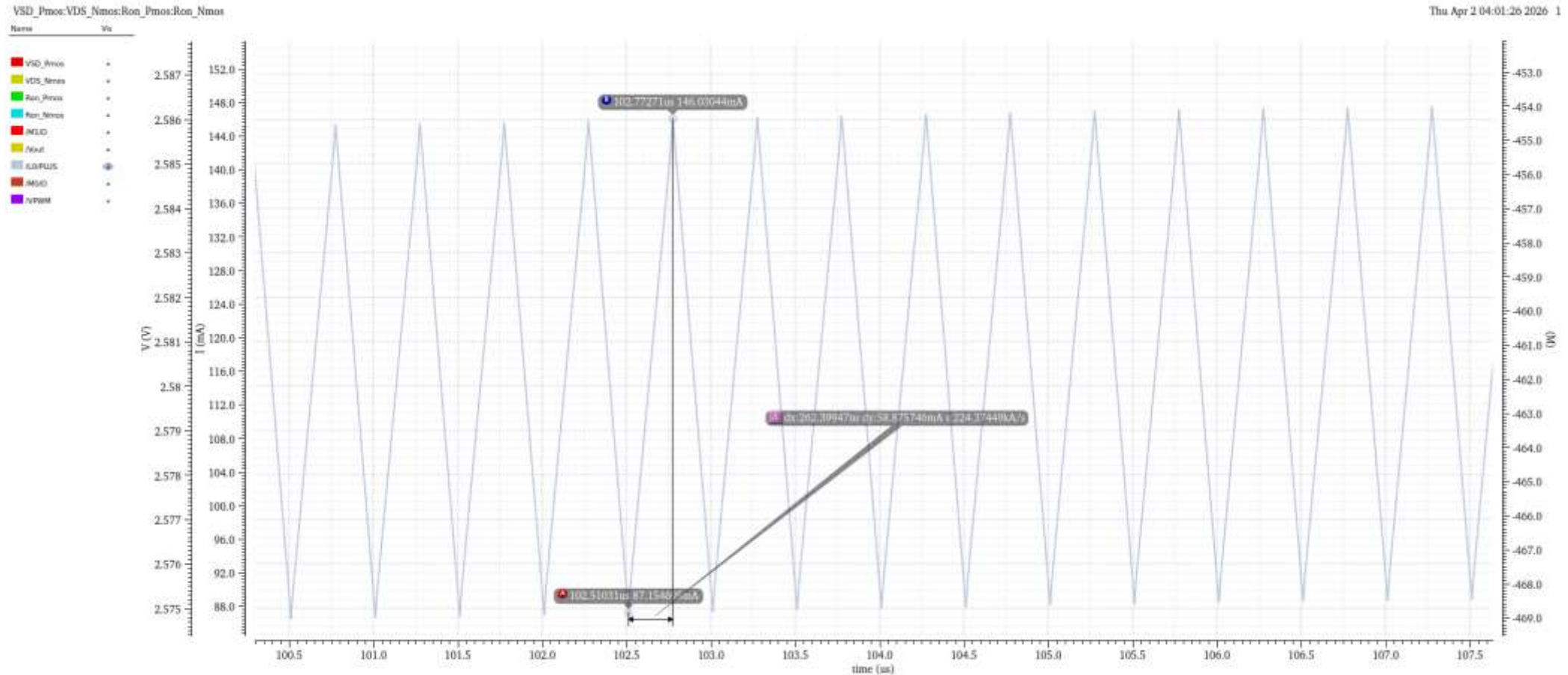16ohm load case (Ron values stay same, I plots change)



16ohm load case

② 16 Ω conduction loss:

$$P_{\text{cond}} = P_{\text{avg}} + P_{\text{ripple}}$$

$$\begin{aligned} P_{\text{avg}} &= I_{\text{avg}}^2 R_{\text{on,pmos}} \text{Duty} + I_{\text{avg}}^2 R_{\text{on,nmos}} (1-\text{Duty}) \\ &= (123.8 \text{ m})^2 (58.28 \text{ m}) (0.36) \\ &\quad + (123.8 \text{ m})^2 (245.4 \text{ m}) (0.64) \\ &= 2.73 \times 10^{-3} \text{ W} \end{aligned}$$

$$\begin{aligned} P_{\text{ripple}} &= I_{\text{ripple}}^2 R_{\text{on,pmos}} \text{Duty} + I_{\text{ripple}}^2 R_{\text{on,nmos}} (1-\text{Duty}) \\ &= (58.79 \text{ m})^2 (58.28 \text{ m}) (0.36) + (58.79 \text{ m})^2 (245.4 \text{ m}) (0.64) \\ &= 6.15 \times 10^{-4} \text{ W} \end{aligned}$$

$$P_{\text{cond}} = P_{\text{avg}} + P_{\text{ripple}} = 3.345 \times 10^{-3} \text{ W}$$

Loss due to average current is dominant.

$$\eta = \frac{P_{\text{tot}} - P_{\text{cond}}}{P_{\text{tot}}} ; P_{\text{tot}} = I_{\text{avg}} \times 1.8 = 0.223 \text{ W}$$

$$\boxed{\eta = 0.98} \quad (\text{increased efficiency as load increases})$$