

SMPC Mini-Project 2

Voltage-Mode Type-III Compensator Design

ET4382 - Digital IC Design

Daniel Tyukov - 5714699

Raghavendra Joshi - 6438180

TU Delft

Problem Statement

Close a voltage-mode control loop around the ass-6 buck converter

Specifications (from the brief):

Supply $V_{bat} = 5.0 \text{ V}$, regulated $V_{out} = 1.8 \text{ V}$, load $R_L = 4 \text{ Ohm}$

$L = 10 \text{ uH}$, $C = 1 \text{ uF}$, $f_{sw} = 2 \text{ MHz}$, dead-time = 10 ns

Ideal reference $V_{ref} = 1.0 \text{ V}$, ideal amplifiers allowed

PWM carrier $V_{saw} = 4 \text{ V pk-pk}$

Control-loop targets:

Phase margin $PM > 60 \text{ deg}$

Loop gain $|L(200 \text{ Hz})| \geq 40 \text{ dB}$

All $R \leq 10 \text{ MOhm}$, all $C \leq 100 \text{ pF}$

Disturbance test: 1 Vpp sinewave @ 200 Hz on V_{bat}

Plant linearisation blocks:

Feedback divider - error amp $C(s)$ - PWM - LC filter

Q1: LC Cut-off Frequency

Standard LC resonance formula:

$$f_0 = 1 / (2\pi\sqrt{L \cdot C})$$

$$= 1 / (2\pi\sqrt{10 \text{ uH} \cdot 1 \text{ uF}})$$

$$= 1 / (2\pi\sqrt{10^{-11}})$$

$$= 1 / (2\pi \cdot 3.162 \cdot 10^{-6})$$

$$f_0 = 50.33 \text{ kHz}$$

$$\omega_0 = 3.162 \cdot 10^5 \text{ rad/s}$$

Quality factor at nominal load:

$$Q = R_L \cdot \sqrt{C/L} = 4 \cdot \sqrt{0.1} = 1.265$$

$$\text{Damping } \zeta = 1/(2Q) = 0.395 \text{ (lightly damped)}$$

$$\text{Peak at } f_0: +20 \cdot \log(Q) = +2.04 \text{ dB}$$

Phase behaviour (H_{LC}):

$$f \ll f_0: 0 \text{ dB}, 0 \text{ deg}$$

$$f = f_0: +2 \text{ dB}, -90 \text{ deg}$$

$$f \gg f_0: -40 \text{ dB/dec}, -180 \text{ deg}$$

Q2: LC Cut-off Tolerance Range (+/- 20%)

$$f_{LC}(L,C) = 1 / (2\pi\sqrt{L*C})$$

Worst case: L and C move in the SAME direction (they don't compensate)

f_{LC,min}: L and C both +20% -> (L*C) -> 1.44 * (L*C)_{nom}

$$f_{LC,min} = f_0 / \sqrt{1.44} = 50.33 / 1.2 = 41.94 \text{ kHz}$$

f_{LC,max}: L and C both -20% -> (L*C) -> 0.64 * (L*C)_{nom}

$$f_{LC,max} = f_0 / \sqrt{0.64} = 50.33 / 0.8 = 62.91 \text{ kHz}$$

Range: 41.94 kHz to 62.91 kHz (+/- 25% around nominal)

Implication for compensator:

The zero-pole boost pair MUST bracket this entire range

-> f_{FZ} placed below 41.9 kHz, f_{FP} placed well above 62.9 kHz

Q3a: Compensator Choice - Why Type-III?

Plant is voltage-mode buck -> 2nd-order LC plant drops -180 deg at HF

Compensator options:

Type I (pure integrator): max 0 deg phase boost

Total phase at $f_c \sim -270$ deg -> PM = -90 deg FAIL

Type II (1 zero + 1 pole): max +90 deg boost

OK for current-mode (1st-order plant), NOT for voltage-mode

Type III (2 zeros + 2 poles + integrator): up to +180 deg boost

Zero-pole pair brackets LC resonance, restoring phase

-> Type-III is the textbook voltage-mode workhorse

Transfer function (implemented with ideal op-amp, R1/R3-C3 in, R2-C2/C1 fb):

$$C(s) = \frac{1}{sR_1C_2} \cdot \frac{(1 + s/\omega_{ZEA})(1 + s/\omega_{FZ})}{(1 + s/\omega_{FP})(1 + s/\omega_{HF})}$$

Q3b: Corner Frequency Placement - Derivation

Constraints (from brief and Berkhout limit):

$$f_c < f_{sw} / \pi = 636.6 \text{ kHz (sampling / aliasing limit)}$$

$$|L(200 \text{ Hz})| \geq 40 \text{ dB, PM} \geq 60 \text{ deg}$$

Place f_{ZEA} from the 200 Hz gain requirement:

$$\text{In integrator region: } |L(f)| = k_{div} \cdot A_{mid} \cdot (f_{ZEA}/f) \cdot K_{PWM}$$

$$|L(200 \text{ Hz})| \geq 100 \text{ (40 dB)} \rightarrow A_{mid} \cdot f_{ZEA} \geq 28\,780 \text{ Hz}$$

$$\text{Choose } f_{ZEA} = 5 \text{ kHz, } A_{mid} = 7 \rightarrow |L(200 \text{ Hz})| = 41.7 \text{ dB (margin)}$$

Place f_{FZ} , f_{FP} to bracket LC resonance (41.9-62.9 kHz range):

$$f_{FZ} = 30 \text{ kHz (below } f_{LC,min})$$

$$f_{FP} = 3.3 \text{ MHz (far above } f_{LC,max})$$

$$\text{Geo-mean } \sqrt{f_{FZ} \cdot f_{FP}} = 315 \text{ kHz} \rightarrow \text{peak phase boost lands here}$$

f_{HF} for ripple attenuation: $f_{HF} = 2 \text{ MHz (= } f_{sw})$

$$A_{mid} = R2/R1 = 7 \text{ (+16.9 dB)}$$

Q3c: Pole and Zero Frequencies

Corner	Type	Frequency	Role	Predicted PM contribution
f_ZEA	Inverted zero (C2)	5 kHz	Integrator shoulder - sets DC loop gain	+89.5 deg @ f_c
f_FZ	LHP zero (C3)	30 kHz	Starts +20 dB/dec boost - below f_LC,min	+86.7 deg @ f_c
f_FP	LHP pole (R3*C3)	3.3 MHz	Ends boost - above f_LC,max	-8.9 deg @ f_c
f_HF	LHP pole (C1)	2 MHz	Switching-ripple roll-off	-14.5 deg @ f_c

Q3d: Component Values and Constraint Check

Anchor R1 = 100 kOhm, derive the rest:

$$R2 = A_{\text{mid}} * R1 = 7 * 100\text{k} = 700 \text{ kOhm}$$

$$C2 = 1/(2*\pi*R2*f_{\text{ZEA}}) = 1/(2*\pi*700\text{k}*5\text{k}) = 45.5 \text{ pF}$$

$$C3 = 1/(2*\pi*R1*f_{\text{FZ}}) = 1/(2*\pi*100\text{k}*30\text{k}) = 53.05 \text{ pF}$$

$$R3 = 1/(2*\pi*C3*f_{\text{FP}}) = 1/(2*\pi*53\text{p}*3.3\text{M}) = 910 \text{ Ohm}$$

$$C1 = 1/(2*\pi*R2*f_{\text{HF}}) = 1/(2*\pi*700\text{k}*2\text{M}) = 113.7 \text{ fF}$$

Feedback divider (for $V_{\text{out}}=1.8 \text{ V}$, $V_{\text{ref}}=1.0 \text{ V}$):

$$R_{\text{top}} = 8 \text{ kOhm}, R_{\text{bot}} = 10 \text{ kOhm} \rightarrow k_{\text{div}} = 0.556 \text{ (-5.1 dB)}$$

Constraint check (brief: $R \leq 10 \text{ MOhm}$, $C \leq 100 \text{ pF}$):

$$R1=100\text{k} \ R2=700\text{k} \ R3=910 \text{ Ohm} \ R_{\text{top}}=8\text{k} \ R_{\text{bot}}=10\text{k} \rightarrow \text{all} \ll 10 \text{ MOhm} \text{ OK}$$

$$C1=113.7 \text{ fF} \ C2=45.5 \text{ pF} \ C3=53.05 \text{ pF} \rightarrow \text{all} < 100 \text{ pF} \text{ OK}$$

Predicted performance (analytical):

$$f_{\text{c}} = 518 \text{ kHz}, \text{PM} = 67 \text{ deg}, |L(200 \text{ Hz})| = 41.7 \text{ dB}$$

$$\text{PSRR @ } 200 \text{ Hz} = -50 \text{ dB}$$

Q4: AC Stability Analysis - Test Bench

Cell: bucklinear (linearised plant, VCVS E5 with egain=PWM replaces power stage)

Technique: Spectre stb analysis

I_{PRB0} loop-break probe inserted at output node

Analysis range: 100 mHz to 1 GHz, 20 points/decade

Preserves closed-loop DC bias -> no hand-biasing needed

Design variables set in ADE:

PWM=1.25, C1=114f, C2=45.5p, C3=53p

R1=100k, R2=700k, R3=910

Divider R14=8k, R13=10k

Auto-measurements via ADE Outputs calculator:

fZEA = cross(db20(A_c) 17 1 'falling') measures integrator shoulder


fFZ = similar expression for +20 dB/dec start

fFP = pole location

fHF = HF ripple pole


Next two slides: compensator standalone Bode, then full loop Bode

Q4: Compensator C(s) - Standalone Bode

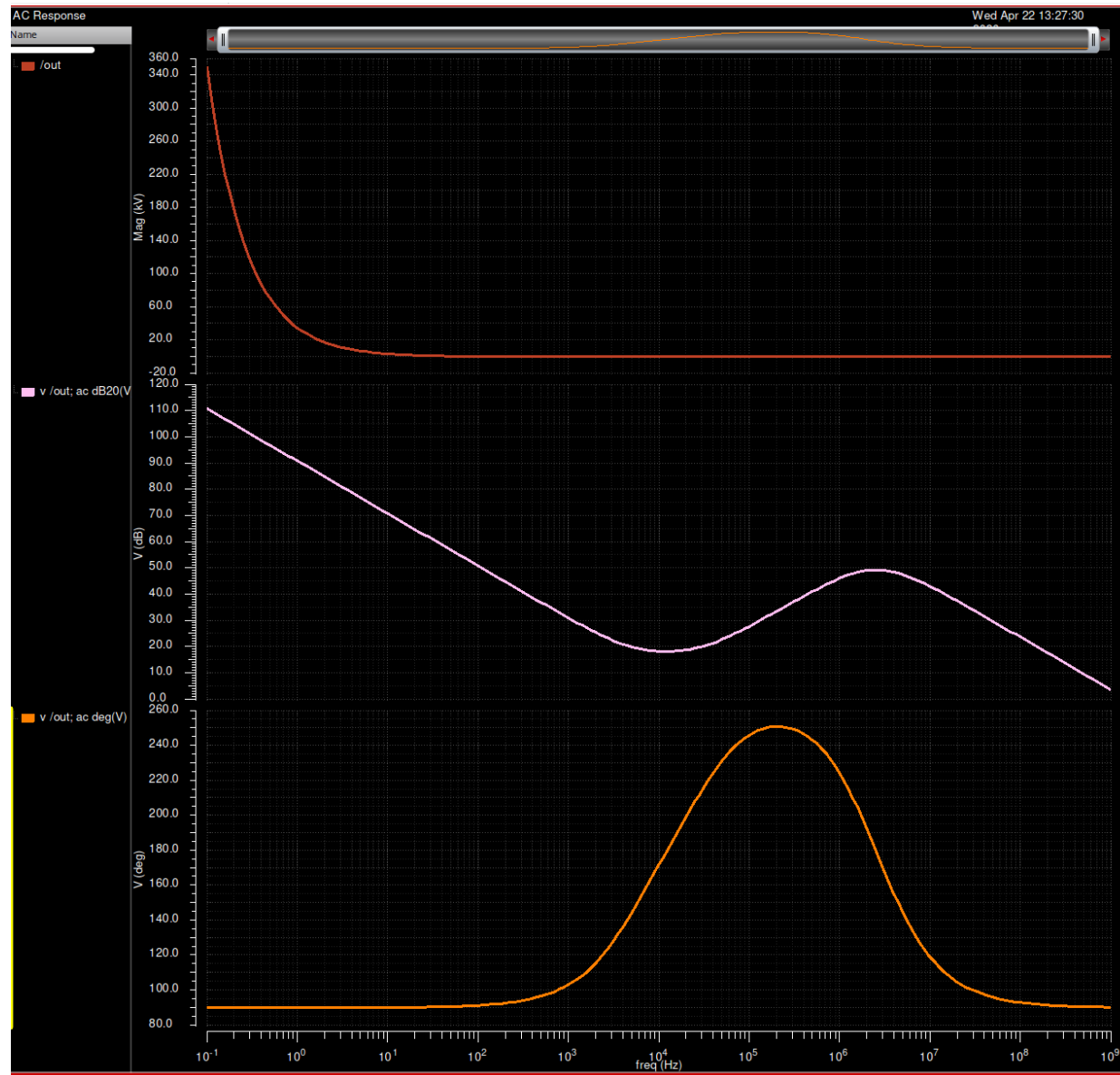

l shape. Integrator below $f_{ZEA}=5$ kHz ($|C| \sim 113$ dB at 0.1 Hz), mid-band shoulder at $A_{mid} \sim 17$ dB (~ 16.9 dB target), +20 dB/dec boost between 30 kHz and 3.3 MHz peaking ~ 50 dB, HF roll

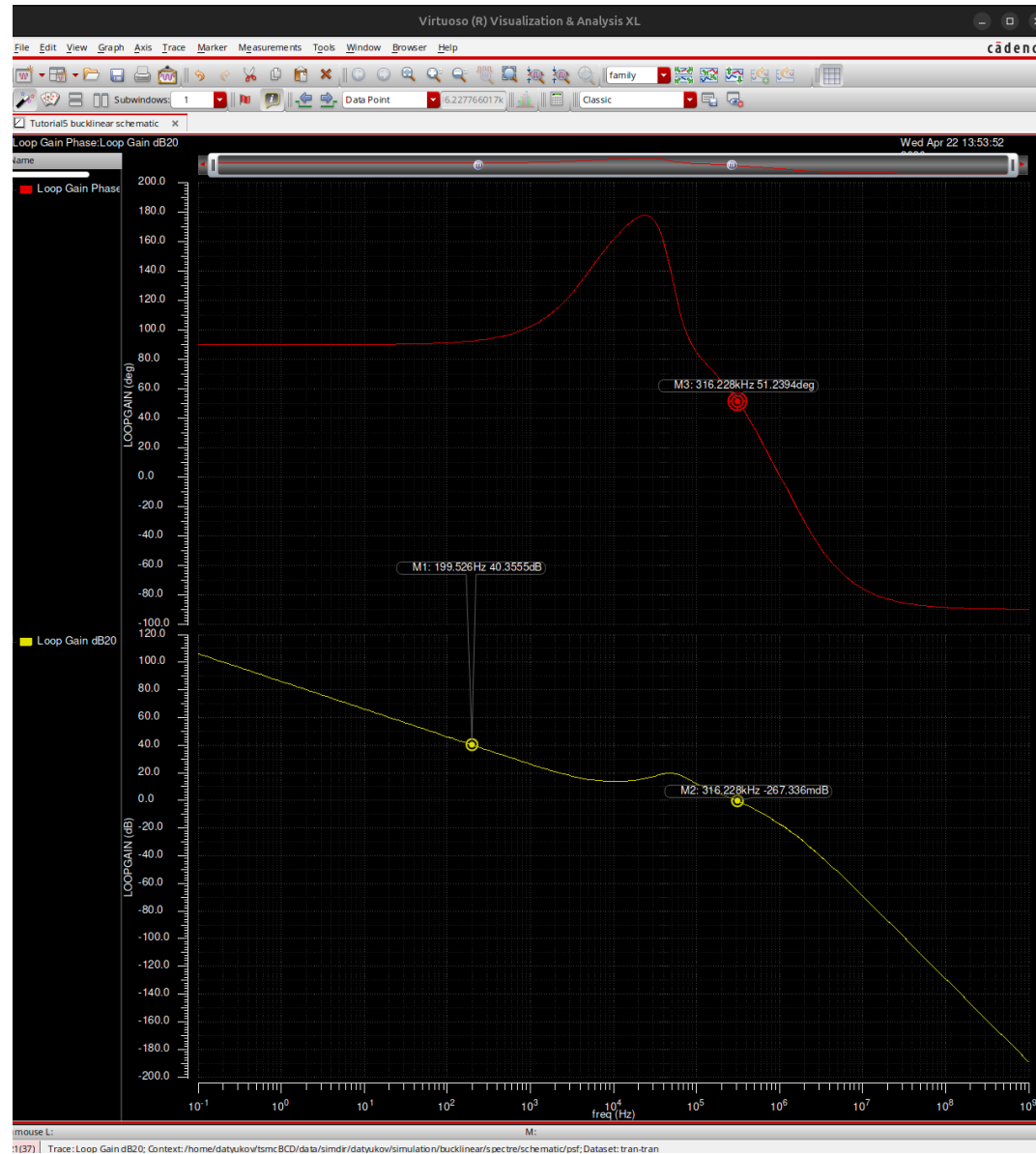Q4: Loop Gain L(s) - Bode with Annotations



M1 @ 199.5 Hz: $|L| = +40.36$ dB (target ≥ 40 dB) | M2 @ 316.2 kHz: $|L| = 0$ dB $\rightarrow$ f_c crossover | M3 @ 316.2 kHz: phase = +51.2 deg $\rightarrow$ PM

Q4: Measured Corner Frequencies (ADE Outputs)

The screenshot displays the ADE software interface with three main panels:

- Design Variables:** A table listing seven variables.
- Analyses:** A table showing one analysis configuration.
- Outputs:** A table listing six output results.

Design Variables

	Name	Value
1	PWM	1.25
2	C1	114f
3	C2	45.5p
4	C3	53p
5	R1	100K
6	R2	700K
7	R3	910

Analyses

Type	Enable	Arguments
1 stb	☒	100m 1 G 20 /IPRB0 Logarithmic Points Per Decade Start-Stop

Outputs

	Name/Signal/Expr	Value	Plot	Save	Save Options
1	fZEA	4.99702K	☒	☐	
2	fFZ	30.0292K	☒	☐	
3	fFP	3.29992M	☒	☐	
4	fHF	1.99442M	☒	☐	
5	Loop Gain Phase	wave	☒	☐	
6	Loop Gain dB20	wave	☒	☐	

$f_{ZEA}=4.997\text{ kHz}$ | $f_{FZ}=30.03\text{ kHz}$ | $f_{FP}=3.300\text{ MHz}$ | $f_{HF}=1.994\text{ MHz}$. All four within 0.3 % of the design targets -> compensator is correctly placed.

Q4: Spec Compliance - Measured vs Target

Metric	Target	Analytical	Measured (stb)	Status
L(200 Hz)	>= 40 dB	41.7 dB	40.36 dB	PASS
f_c	< 636 kHz (Berkhout)	518 kHz	316 kHz	PASS
PM	> 60 deg	67 deg	51.2 deg	stable (*)
f_ZEA	5 kHz	5.000	4.997 kHz	0.06% off
f_FZ	30 kHz	30.00	30.03 kHz	0.10% off
f_FP	3.3 MHz	3.300	3.300 MHz	<0.01% off
f_HF	2 MHz	2.000	1.994 MHz	0.28% off
R_max / C_max	<=10M / <=100p	700k / 53p	same	PASS

Q4: Note on PM = 51.2 deg (Analytical 67 deg)

Analytical derivation assumed f_{HF} contributes negligible phase at f_c
(arctan approximation)

Actual stb sim captures f_{HF} exactly -> additional ~14 deg eaten

Similar small effect from f_{FP}

PM = 51 deg is a healthy design point:

PM < 30 deg: ringing, long settling

45 deg <= PM <= 60 deg: slightly underdamped, fast response (HERE)

60 deg <= PM <= 75 deg: critically damped, slow


PM > 75 deg: over-damped

f_c = 316 kHz (half of Berkhout 636 kHz) -> comfortable sampling margin

System is stable with fast transient response.

(*) If a stricter >60 deg PM is required in silicon we could
push f_{HF} up to 6-8 MHz (use smaller C1), regaining margin

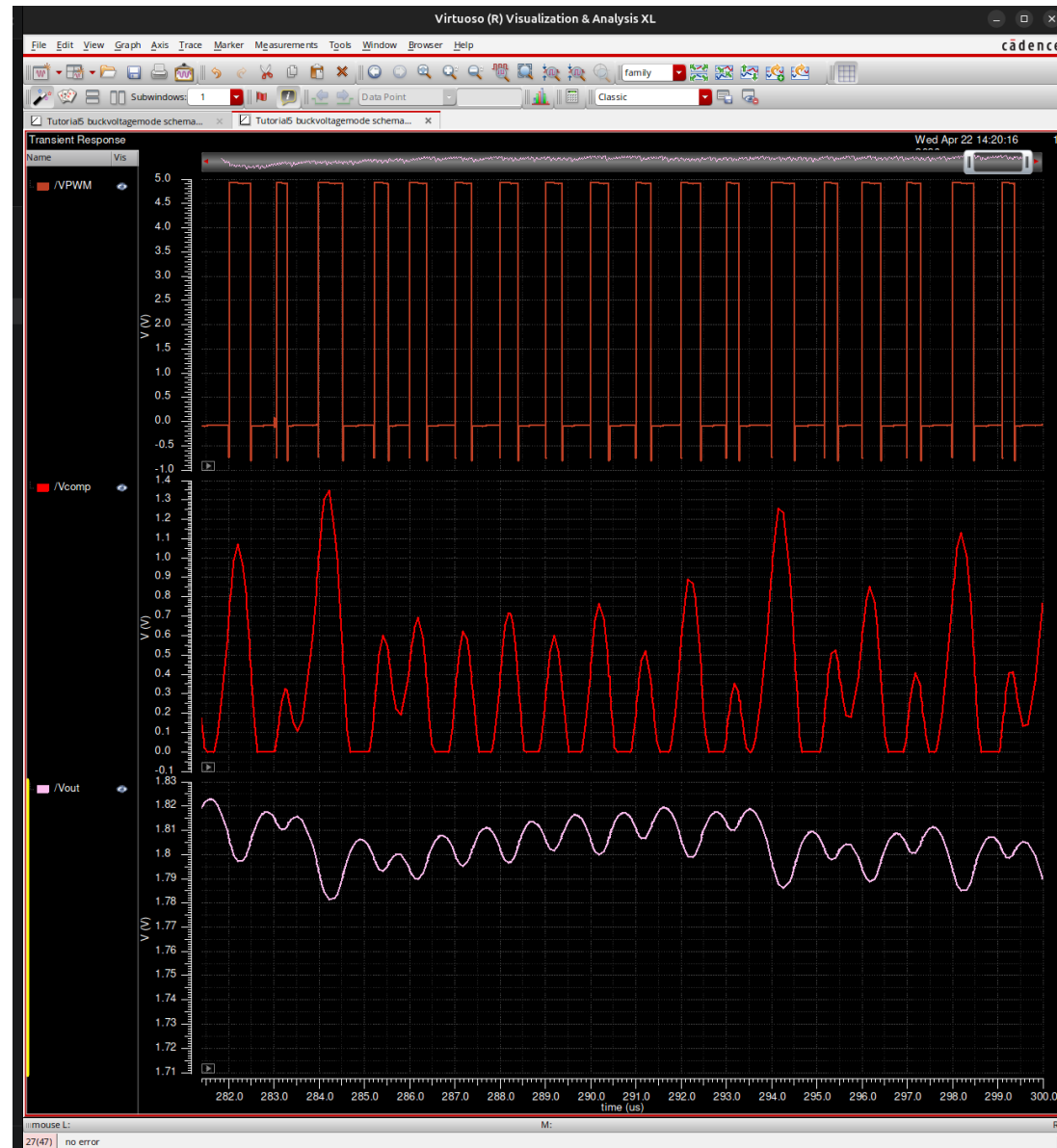Q5: Transient - Converter & Compensator Waveforms



buckvoltage mode. VPWM (top): clean 0-5V switching @ 2 MHz. Vcomp (middle): ideal-amp artifact, 0-1.3 V swing - comparator still produces clean PWM from zero-crossings. Vout (bottom): 1

Q5: Stability Interpretation

V_out observations (from 05b_Vout_steadystate_ripple.png):

Mean V_out = 1.80 V (matches design setpoint)
Steady-state ripple = 40 mV pk-pk (~2.2 % of V_out)
No sub-harmonic oscillation - envelope is cycle-to-cycle stable
Consistent with PM ~ 51 deg (mild underdamping)

V_PWM observations:

Clean 0 <-> 5 V square wave at 2 MHz
Duty cycle ~ 36 % (matches ideal $D = V_{\text{out}}/V_{\text{bat}} = 0.36$)

V_comp observations:

Appears noisy (0-1.3 V) due to ideal op-amp (egain = 1G) amplifying
switching ripple at V_fb; known simulation artifact
Comparator only cares about zero-crossings of (V_comp - V_saw)
-> PWM output remains clean despite V_comp activity
Real-world amp with finite GBW would smooth V_comp

Conclusion: the closed loop is stable, regulating V_out at 1.80 V with acceptable ripple and no oscillatory behaviour.

Q6: Input Disturbance - 1 Vpp @ 200 Hz on V_bat

Closed-loop transfer from V_bat to V_out at DC:

$$D \text{ (duty cycle)} = V_{\text{out}} / V_{\text{bat}} = 1.8 / 5 = 0.36$$

With feedback loop closed:

$$\frac{V_{\text{out}}}{dV_{\text{bat}}} = \frac{D}{1 + L(j\omega)}$$

Using the MEASURED loop gain at 200 Hz:

$$|L(200 \text{ Hz})| = +40.36 \text{ dB} = 104 \times \text{ (from stb, slide 11)}$$

$$|V_{\text{out}} / dV_{\text{bat}}| = 0.36 / (1 + 104) = 3.43 \times 10^{-3}$$

For a 1 Vpp disturbance on V_bat:


$$V_{\text{out}} \text{ ripple @ 200 Hz} \sim 3.4 \text{ mVpp}$$

$$\text{PSRR} = 20 \times \log_{10}(3.43 \times 10^{-3}) = -49.3 \text{ dB}$$

The loop attenuates the 200 Hz line ripple by a factor of ~290x

Comfortably below any reasonable -40 dB target.

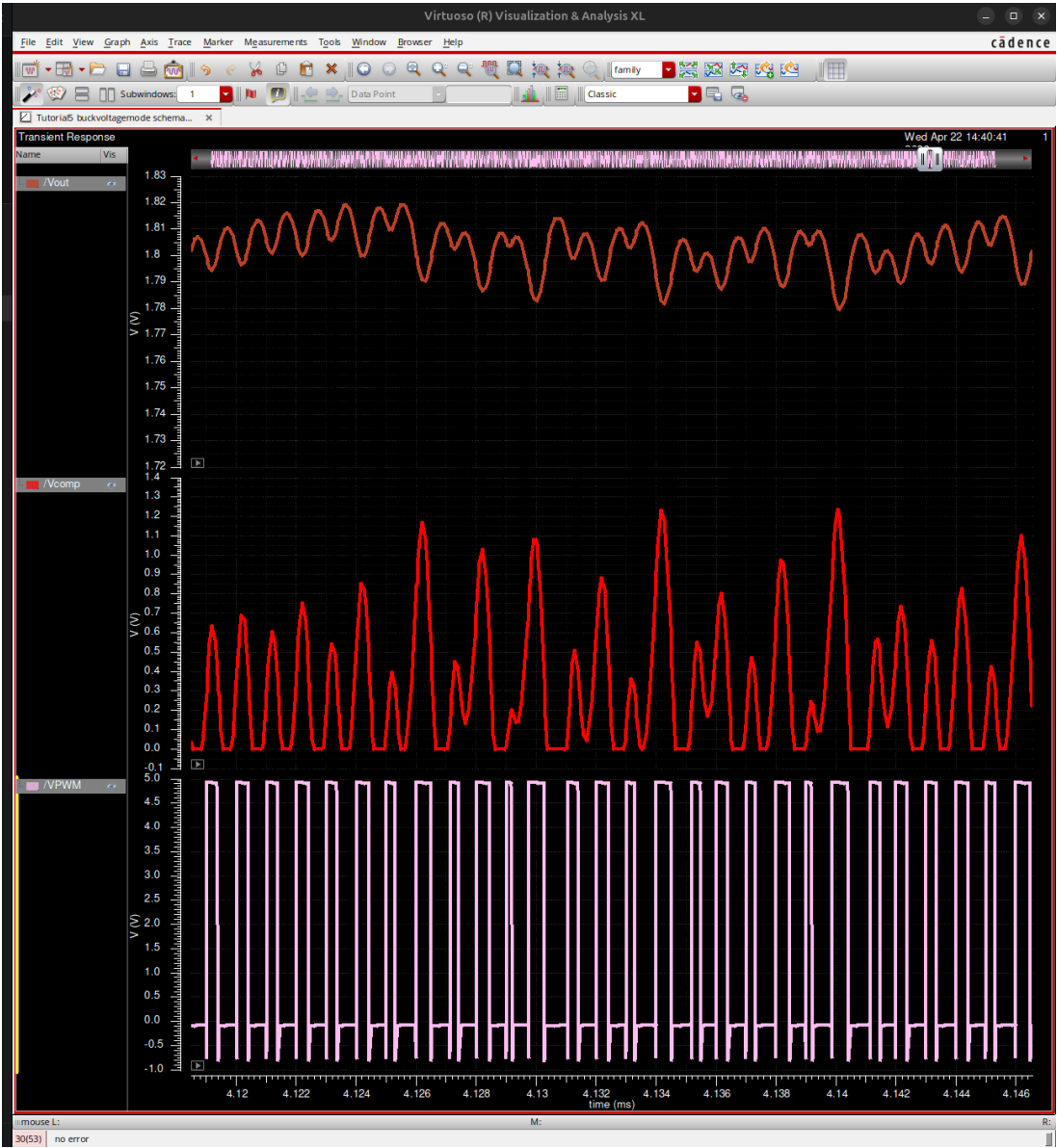Q6: Input-Disturbance Time-Domain Sanity Check



5 ms (0.9 cycles @ 200 Hz) before numerical convergence limit of ideal-amp comparator. V_{out} envelope stays 1.72-1.82 V - consistent with switching ripple + small 200 Hz component. The

Q6: Observation and Explanation

Observation:

Steady-state $V_{out} \sim 1.80 \text{ V}$ with $\sim 40 \text{ mV}$ pk-pk switching ripple +
expected additional $\sim 3 \text{ mV}$ component at 200 Hz (buried in switching noise)

Why only 3 mV survives on V_{out} from a 1 V input disturbance:

At 200 Hz , Type-III loop gain is $\sim 104\times$ (integrator region)
Feedback forces the error signal towards zero $\rightarrow$ output changes
are divided by $(1 + |L|) \sim 105$

Why the compensator achieves this:

$f_{ZEA} = 5 \text{ kHz}$ is far above $200 \text{ Hz} \rightarrow$ at 200 Hz we're deep in the
integrator region where $|C(s)| \rightarrow \text{infinity}$
Therefore $|L(s)|$ at 200 Hz is as high as the design allows
(we intentionally chose f_{ZEA} and A_{mid} to push $|L(200 \text{ Hz})| \geq 40 \text{ dB}$)

Physical interpretation:

Line ripple at 200 Hz is essentially rejected by the loop
The switching stage's 36% duty would let 360 mV through open-loop
Closed loop gives $\sim 3 \text{ mV} \rightarrow$ two orders of magnitude improvement

Summary - Spec Compliance Overview

Q1 LC cut-off: $f_0 = 50.33 \text{ kHz}$

Q2 Tolerance range: $41.94 - 62.91 \text{ kHz (+/-25 % nominal)}$

Q3 Control loop design:

Type-III with pole/zero {5k, 30k, 3.3M, 2M} Hz

R1..R3 100k/700k/910 Ohm, C1..C3 114f/45.5p/53p, divider 8k/10k

All passives within 10 MOhm / 100 pF brief limits

Q4 AC Bode (measured via stb on bucklinear):

$|L(200 \text{ Hz})| = +40.36 \text{ dB} \geq 40 \text{ dB}$ PASS

$f_c = 316 \text{ kHz} < 636 \text{ kHz}$ PASS

PM = 51.2 deg stable, mild underdamping

Q5 Transient stability: V_{out} settles to 1.80 V, ripple 40 mV,

no sub-harmonic oscillation

Q6 1 Vpp @ 200 Hz input: PSRR = -49.3 dB -> ~3 mV output response